

Lab session-5

Learning Outcomes:

- a) Designing a 32-bit register file for a MIPS processor,
- b) Clock gating and integration of components.

Designing a 32-bit register file

Register File parameters

Width of each Registers- 32-bit;

No. of input ports- six;

- Three ports for addresses
- One port for data
- One for clock, one for *RegWrite*

no. of output ports= two;

Register file is comprised of following modules,

- (a) **D-FF**,
- (b) **Decoder** and,
- (c) **Multiplexer**

Designing a 32-bit Register using D-FF

Functional Requirements are

1. Control input C
2. Data input D

generate

genvar i ;

generate

for($i = 0$; $i < N$; $i = i + 1$)

begin DFF D1(\dots);

end

endgenerate

Pseudo-code for the register

-Parallel in parallel out type

input $clk, clear$;

input[31 : 0] pi ;

output reg [31 : 0] po ;

always @ (*posedge* clk)

begin

if (clr) $po \leq 32'h0000$;


else $po \leq pi$;

end

Design of Decoder

A *Decoder* should

 - (a) *select registers* as per the input register number
- (b) be enabled (*en*)



Pseudo-code for decoder

```
always @(en, in)
begin if (en) out = 8'b0;
else case(in)
begin
2'b00 : out[0] = 1'b1;
2'b01 : out[1] = 1'b1;
2'b10 : out[2] = 1'b1;
2'b11 : out[3] = 1'b1;
default : out =
endcase
end
```

Design of the Multiplexor

Pseudo-code for Mux

```
input [1 : 0] regno
input [31 : 0] a0, a1, ...;
output[31 : 0] outmux;
always @ (*) begin
  case(regno)
    2'b00 : outmux = a0;
    2'b01 : outmux = a1;
    2'b10 : outmux = a2;
    2'b11 : outmux = a3;
    default : out
  endcase
end
```

Remark:

- case statements should have a *default* condition.
- if statements should have a corresponding *else*.

Definition of ICG

ICG, otherwise known as **I**ntegrated **C**lock **G**ating cell is placed to **have power saving**.

Pseudo-Code of ICG

```
module(...)
reg — clk, reg — write, decoder — out;
output gated — clk;
and(gated — clk, reg — clk, reg — write, decoder — out)
endmodule
```

Modularity increases *re – usability* and reduces the time for bug-fixes.

Integrate the following modules:

- (A) *Decoder* [5 : 32]
- (B) *Mux* [32:1]
- (C) *Registers* 32-bit [32]
- (D) *ICG*